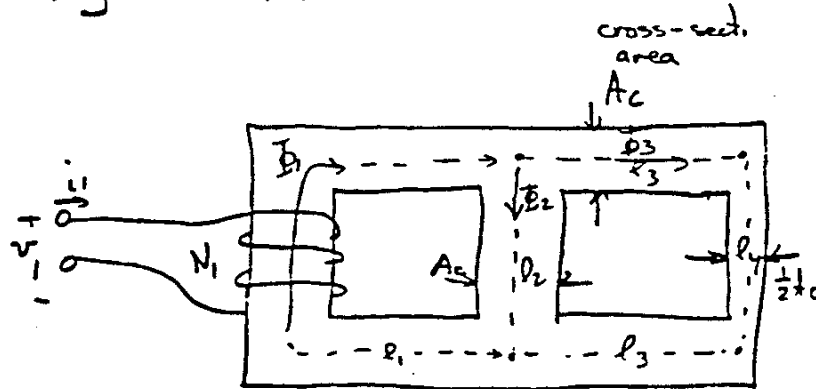


Solution to Problem 12.1

Magnetic Circuits




$$\mu = 1000\mu_0$$

$$\mu_0 = 4\pi \cdot 10^{-7} \text{ H/m}$$

$$N_1 = 10 \text{ turns}$$

(a) Equivalent magnetic circuit

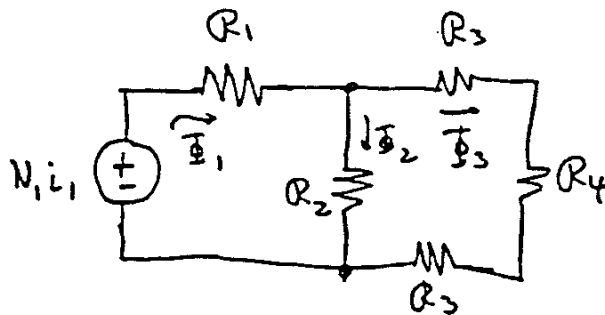

where

$$R_1 = \frac{l_1}{\mu A_c} = \frac{(9 \text{ cm}) (100 \text{ cm/m})}{(4\pi \cdot 10^{-4} \text{ H/m}) (1 \text{ cm}^2)} = 7.16 \cdot 10^5 \text{ H}^{-1}$$

$$R_2 = \frac{l_2}{\mu A_c} = \frac{(3 \text{ cm}) (100 \text{ cm/m})}{(4\pi \cdot 10^{-4} \text{ H/m}) (1 \text{ cm}^2)} = 2.39 \cdot 10^5 \text{ H}^{-1}$$

$$R_3 = \frac{l_3}{\mu A_c} = R_2 = 2.39 \cdot 10^5 \text{ H}^{-1}$$

$$R_4 = \frac{l_4}{\mu \cdot \frac{1}{2} A_c} = \frac{(3 \text{ cm}) (100 \text{ cm/m})}{(4\pi \cdot 10^{-4} \text{ H/m}) (0.5 \text{ cm}^2)} = 4.77 \cdot 10^5 \text{ H}^{-1}$$

(1)

Total reluctance of right leg

$$R_r = 2R_3 + R_4 = 9.56 \cdot 10^5 \text{ H}^{-1}$$

b) Determine inductance of winding

1st, determine Φ_1 . From the magnetic circuit, we have

$$\Phi_1 = \frac{N_1 i_1}{R_1 + (R_2 \parallel R_r)}$$


From Faraday's law,

$$v_1 = N_1 \frac{d\Phi_1}{dt} = \frac{N_1^2}{R_1 + (R_2 \parallel R_r)} \frac{di_1}{dt}$$


Hence, $v_1 = L_1 \frac{di_1}{dt}$ with $L_1 = \frac{N_1^2}{R_1 + (R_2 \parallel R_r)}$

$$\Rightarrow L_1 = \frac{(10)^2}{(7.16 \cdot 10^5) + (2.39 \cdot 10^5) \parallel (9.56 \cdot 10^5)} = 110 \mu\text{H}$$

A second winding is added;

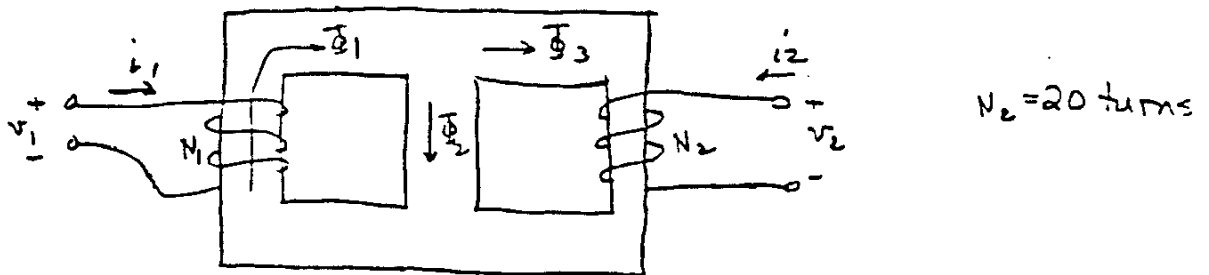

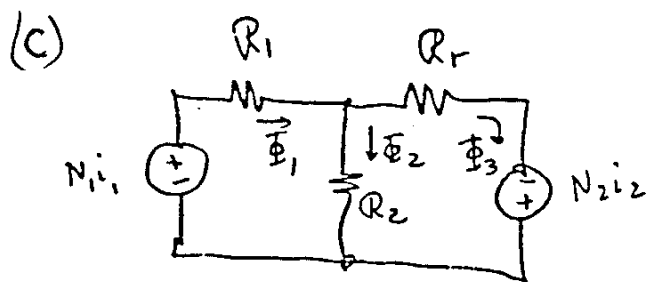Note direction of wire in second winding, and defined direction of i_2 . Just as i_1 tends to increase Φ_1 , i_2 tends to increase (rather than decrease) Φ_3 . The magnetic circuit is



note polarity of magnetomotive force N .

(d) Express electrical equations for this magnetic circuit in the form

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} L_{11} & L_{12} \\ L_{12} & L_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\text{so } v_1 = N_1 \dot{\Phi}_1 = L_{11} \dot{i}_1 + L_{12} \dot{i}_2 \quad (1^{\text{st}} \text{ line})$$

$$\Rightarrow \Phi_1 = \frac{L_{11}}{N_1} i_1 + \frac{L_{12}}{N_1} i_2$$


$$\Rightarrow L_{11} = \left. \frac{N_1 \Phi_1}{i_1} \right|_{i_2=0}, \quad L_{12} = \left. \frac{N_1 \Phi_1}{i_2} \right|_{i_1=0}$$

$$\text{likewise, } v_2 = N_2 \dot{\Phi}_3 = L_{12} \dot{i}_1 + L_{22} \dot{i}_2 \quad (2^{\text{nd}} \text{ line})$$

$$\Rightarrow \Phi_3 = \frac{L_{12}}{N_2} i_1 + \frac{L_{22}}{N_2} i_2$$

$$\Rightarrow L_{12} = \left. \frac{N_2 \Phi_3}{i_1} \right|_{i_2=0}, \quad L_{22} = \left. \frac{N_2 \Phi_3}{i_2} \right|_{i_1=0}$$

(i) when $i_2 = 0$, we have

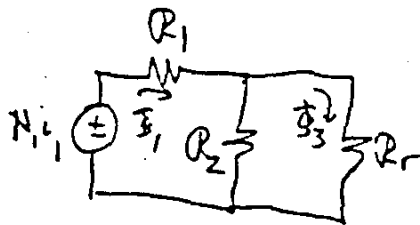


$$\left. \begin{aligned} \Phi_1 &= \frac{N_1 i_1}{R_1 + R_2 \parallel R_r} \\ \Rightarrow L_{11} &= \frac{N_1^2}{R_1 + R_2 \parallel R_r} \\ &= 110 \mu\text{H} \end{aligned} \right\} \begin{array}{l} \text{as for } L_{11} \\ \text{in part} \\ \text{(b)} \end{array}$$

$$\Phi_3 = N_1 i_1 \frac{R_2 \parallel R_r}{R_1 + R_2 \parallel R_r} \cdot \frac{1}{R_r}$$

$$R_2 \parallel R_r = 1.71 \cdot 10^5$$

$$\Rightarrow L_{12} = \frac{N_1 N_2}{R_1 + R_2 \parallel R_r} \cdot \frac{R_2 \parallel R_r}{R_r} = 44 \mu\text{H}$$

(ii) when $i_1 = 0$, we have

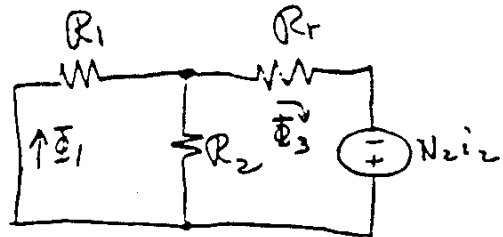

$$\Phi_3 = N_2 i_2 \cdot \frac{1}{R_r + R_1 \parallel R_2} \Rightarrow L_{22} = \frac{N_2^2}{R_r + R_1 \parallel R_2} = 352 \mu\text{H}$$

check:

$$\Phi_1 = N_2 i_2 \cdot \frac{R_1 \parallel R_2}{R_r + R_1 \parallel R_2} \cdot \frac{1}{R_1}$$

$$\Rightarrow L_{12} = \frac{N_1 N_2}{R_r + R_1 \parallel R_2} \cdot \frac{R_1 \parallel R_2}{R_1} = 44 \mu\text{H} \checkmark$$

so

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} 110 \mu\text{H} & 44 \mu\text{H} \\ 44 \mu\text{H} & 352 \mu\text{H} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$